

**Problems of Electric circuits**

---

1) A charge of 920 C was passed through a wire in 5 minutes. Calculate the average electric current during that interval.

*Answer:* 3.07 A.

2) How long does it take for 2320 C to pass a given point in a wire that carries an electric current of 3.7 A?

*Answer:* 627 s.

3) Find the resistance of a resistor through which 2520 C flow in 21 minutes if the potential difference across it is 8 V.

*Answer:* 4 Ω.

4) Find the electric resistance of an aluminium rod 38 m long, if its cross-sectional area is 0.3 mm<sup>2</sup> and its resistivity is 2.82×10<sup>-8</sup> Ω·m.

*Answer:* 3.57 Ω.

5) Calculate the resistivity of a wire 26 m long, if its cross-sectional area is 2.4 mm<sup>2</sup> and its electric resistance is 1.26 Ω.

*Answer:* 1.16×10<sup>-7</sup> Ω·m.

6) Calculate the electric resistance of a silver wire 1.4 mm in diameter and 48 m long if its resistivity is 1.57×10<sup>-8</sup> Ω·m.

*Answer:* 0.488 Ω.

7) A battery with an emf (electromotive force) of 8 V delivers 110 mA to a 72 Ω load.

a) What is the internal resistance of the battery?

b) What is its terminal potential difference when joined to this load?

*Answer:* a) 0.7 Ω, b) 7.923 V.

8) A 47 μF capacitor is charged to a potential difference of 52 V. Find the charge on the capacitor.


*Answer:* 2.444 mC.

9) For the circuit shown below, the resistors are  $R_1 = 22 \Omega$  and  $R_2 = 26 \Omega$ . The circuit applied voltage is  $V_A - V_B = 18 \text{ V}$ . Find:

a) The circuit's total resistance.

b) Current flowing through resistor  $R_2$ .

c) The voltage across  $R_2$ .

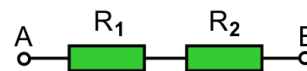


*Answer:* a) 48 Ω, b) 0.375 A, c) 9.75 V.

**Problems of Electric circuits**

10) For the circuit shown below, the resistors are  $R_1 = 27 \Omega$  and  $R_2 = 25 \Omega$ . The circuit applied voltage is  $V_A - V_B = 18 \text{ V}$ . Find:

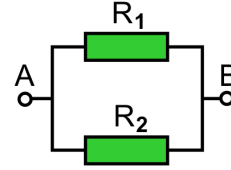- a) The circuit's total resistance.
- b) Current flowing through resistor  $R_2$ .
- c) The voltage across  $R_2$ .


Answer: a)  $12.98 \Omega$ , b)  $0.72 \text{ A}$ , c)  $18 \text{ V}$ .



11) For the circuit shown below, the resistors are  $R_1 = 19 \Omega$ ,  $R_2 = 16 \Omega$  and  $R_3 = 29 \Omega$ . The circuit applied voltage is  $V_A - V_B = 45 \text{ V}$ . Find:

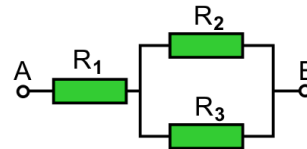- a) The circuit's total resistance.
- b) Current flowing through resistor  $R_2$ .
- c) The voltage across  $R_2$ .


Answer: a)  $29.31 \Omega$ , b)  $0.9894 \text{ A}$ , c)  $15.83 \text{ V}$ .



12) For the circuit shown below, the resistors are  $R_1 = 2 \Omega$ ,  $R_2 = 18 \Omega$  and  $R_3 = 9 \Omega$ . The circuit applied voltage is  $V_A - V_B = 29 \text{ V}$ . Find:

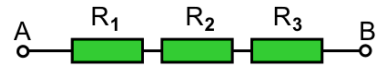- a) The circuit's total resistance.
- b) Current flowing through resistor  $R_2$ .
- c) The voltage across  $R_2$ .


Answer: a)  $29 \Omega$ , b)  $1 \text{ A}$ , c)  $18 \text{ V}$ .



13) For the circuit shown below, the resistors are  $R_1 = 17 \Omega$ ,  $R_2 = 7 \Omega$  and  $R_3 = 13 \Omega$ . The circuit applied voltage is  $V_A - V_B = 27 \text{ V}$ . Find:

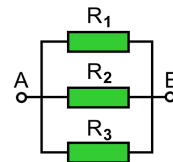- a) The circuit's total resistance.
- b) Current flowing through resistor  $R_2$ .
- c) The voltage across  $R_2$ .


Answer: a)  $3.589 \Omega$ , b)  $3.857 \text{ A}$ , c)  $27 \text{ V}$ .



14) For the circuit shown below, the resistors are  $R_1 = 6 \Omega$ ,  $R_2 = 11 \Omega$  and  $R_3 = 11 \Omega$ . The circuit applied voltage is  $V_A - V_B = 39 \text{ V}$ . Find:

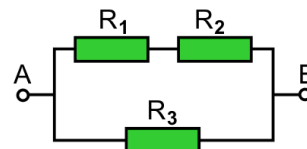- a) The circuit's total resistance.
- b) Current flowing through resistor  $R_2$ .
- c) The voltage across  $R_2$ .


Answer: a)  $6.679 \Omega$ , b)  $2.294 \text{ A}$ , c)  $25.24 \text{ V}$ .



**Problems of Electric circuits**

15) For the circuit shown below, the resistors are  $R_1 = 14 \Omega$ ,  $R_2 = 25 \Omega$ ,  $R_3 = 24 \Omega$  and  $R_4 = 8 \Omega$ . The circuit applied voltage is  $V_A - V_B = 9 \text{ V}$ . Find:

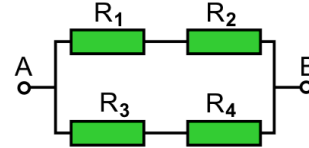
- a) The circuit's total resistance.
- b) Current flowing through resistor  $R_2$ .
- c) The voltage across  $R_2$ .



Answer: a)  $17.58 \Omega$ , b)  $0.2308 \text{ A}$ , c)  $5.769 \text{ V}$ .

16) For the circuit shown below the capacitances are  $C_1 = 19 \mu\text{F}$ ,  $C_2 = 5 \mu\text{F}$  and  $C_3 = 16 \mu\text{F}$ . The circuit applied voltage is  $V_A - V_B = 11 \text{ V}$ . Find:

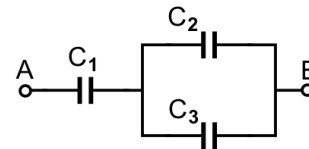
- a) Circuit's equivalent capacitance.
- b) Charge stored on capacitor  $C_2$ .
- c) Potential difference across  $C_2$ .



Answer: a)  $9.975 \mu\text{F}$ , b)  $26.13 \mu\text{C}$ , c)  $5.225 \text{ V}$ .

17) For the circuit shown below the capacitances are  $C_1 = 4 \mu\text{F}$ ,  $C_2 = 11 \mu\text{F}$  and  $C_3 = 7 \mu\text{F}$ . The circuit applied voltage is  $V_A - V_B = 16 \text{ V}$ . Find:

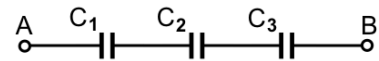
- a) Circuit's equivalent capacitance.
- b) Charge stored on capacitor  $C_2$ .
- c) Potential difference across  $C_2$ .



Answer: a)  $2.067 \mu\text{F}$ , b)  $33.07 \mu\text{C}$ , c)  $3.007 \text{ V}$ .

18) For the circuit shown below the capacitances are  $C_1 = 9 \mu\text{F}$ ,  $C_2 = 27 \mu\text{F}$  and  $C_3 = 11 \mu\text{F}$ . The circuit applied voltage is  $V_A - V_B = 24 \text{ V}$ . Find:

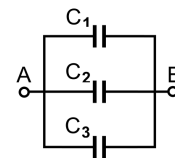
- a) Circuit's equivalent capacitance.
- b) Charge stored on capacitor  $C_2$ .
- c) Potential difference across  $C_2$ .



Answer: a)  $47 \mu\text{F}$ , b)  $648 \mu\text{C}$ , c)  $24 \text{ V}$ .

19) For the circuit shown below the capacitances are  $C_1 = 28 \mu\text{F}$ ,  $C_2 = 7 \mu\text{F}$  and  $C_3 = 20 \mu\text{F}$ . The circuit applied voltage is  $V_A - V_B = 14 \text{ V}$ . Find:

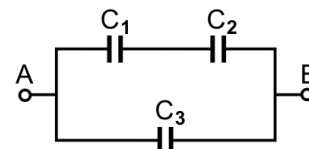- a) Circuit's equivalent capacitance.
- b) Charge stored on capacitor  $C_2$ .
- c) Potential difference across  $C_2$ .




Answer: a)  $25.6 \mu\text{F}$ , b)  $78.4 \mu\text{C}$ , c)  $11.2 \text{ V}$ .

**Problems of Electric circuits**

20) For the circuit shown below the capacitances are  $C_1 = 11 \mu\text{F}$ ,  $C_2 = 26 \mu\text{F}$ ,  $C_3 = 15 \mu\text{F}$  and  $C_4 = 25 \mu\text{F}$ . The circuit applied voltage is  $V_A - V_B = 5 \text{ V}$ . Find:

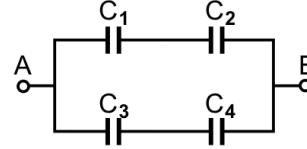
- a) Circuit's equivalent capacitance.
- b) Charge stored on capacitor  $C_2$ .
- c) Potential difference across  $C_2$ .



Answer: a)  $17.1 \mu\text{F}$ , b)  $38.65 \mu\text{C}$ , c)  $1.486 \text{ V}$ .

21) For the circuit shown below the capacitances are  $C_1 = 22 \mu\text{F}$ ,  $C_2 = 16 \mu\text{F}$ ,  $C_3 = 10 \mu\text{F}$ ,  $C_4 = 19 \mu\text{F}$  and  $C_5 = 2 \mu\text{F}$ . The circuit applied voltage is  $V_A - V_B = 45 \text{ V}$ . Find:

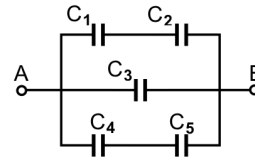
- a) Circuit's equivalent capacitance.
- b) Charge stored on capacitor  $C_2$ .
- c) Potential difference across  $C_2$ .



Answer: a)  $21.07 \mu\text{F}$ , b)  $416.8 \mu\text{C}$ , c)  $26.05 \text{ V}$ .

22) For the circuit shown below the capacitances are  $C_1 = 16 \mu\text{F}$  and  $C_2 = 18 \mu\text{F}$ . The circuit applied voltage is  $V_A - V_B = 38 \text{ V}$ . Find:

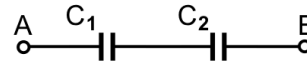- a) Circuit's equivalent capacitance.
- b) Charge stored on capacitor  $C_2$ .
- c) Potential difference across  $C_2$ .



Answer: a)  $8.471 \mu\text{F}$ , b)  $321.9 \mu\text{C}$ , c)  $17.88 \text{ V}$ .

23) A light bulb has an operating potential difference of  $40 \text{ V}$  and draws a current of  $5 \text{ A}$ . Calculate its power rating and its resistance.

Answer:  $200 \text{ W}$ ,  $8 \Omega$ .

24) How much does it cost to operate a  $17 \text{ W}$  light bulb for 16 days if electrical energy costs  $0.112 \text{ \$}$  per  $\text{kW}\cdot\text{h}$ ?

Answer:  $0.73 \text{ \$}$ .

25) A  $73 \text{ W}$  lamp is operated for 15 hours a day. How much energy does it take to operate the lamp for 27 days? Express your answer in joules and kilowatt-hours.

Answer:  $1.064 \times 10^8 \text{ J}$ ,  $29.57 \text{ kW}\cdot\text{h}$ .

26) A resistor is rated at  $870 \text{ W}$  and its electrical resistance is  $1040 \Omega$ .

- a) What is the maximum voltage that can be applied across the resistor?
- b) What is the current at this voltage?

Answer: a)  $951.2 \text{ V}$ , b)  $914.6 \text{ mA}$ .

## Problems of Electric circuits

---

27) Three resistors,  $45\ \Omega$ ,  $57\ \Omega$ , and  $68\ \Omega$ , are connected in series across a battery that provides  $24\ \text{V}$ .

- a) Calculate the voltage across each resistor.
- b) Calculate the power dissipated in each resistor.

Answer: a)  $6.35\ \text{V}$ ,  $8.05\ \text{V}$ ,  $9.6\ \text{V}$ , b)  $0.897\ \text{W}$ ,  $1.14\ \text{W}$ ,  $1.36\ \text{W}$ .

28) Two resistors,  $23\ \Omega$  and  $30\ \Omega$ , are connected in parallel. If the current through the  $23\ \Omega$  resistor is  $4\ \text{A}$ , find:

- a) The current in the other resistor.
- b) The total power consumed by the two resistors.

Answer: a)  $3.07\ \text{A}$ , b)  $650\ \text{W}$ .

29) Find the electric potential drop across a  $92\ \text{W}$  resistor that draws a current of  $250\ \text{mA}$ .

Answer:  $368\ \text{V}$ .

30) A  $55\ \text{W}$  electric lamp draws a current of  $4.1\ \text{A}$ . Find the voltage applied and the resistance of the lamp.

Answer:  $13.4\ \text{V}$ ,  $3.27\ \Omega$ .

31) An  $196\ \text{nF}$  capacitor is charged with  $153.9\ \mu\text{C}$ . Find the voltage and the energy stored.

Answer:  $785\ \text{V}$ ,  $60.39\ \text{mJ}$ .

32) A capacitor is connected across a  $750\ \text{V}$  supply. If the energy stored is  $29.53\ \text{J}$ , find:

- a) The capacitance of the capacitor.
- b) The charge on the capacitor.

Answer: a)  $105\ \mu\text{F}$ , b)  $78.75\ \text{mC}$ .

33) a) Calculate the energy stored in an  $130\ \mu\text{F}$  capacitor when charged to  $460\ \text{V}$ .

b) Find also the charge on the capacitor.

Answer: a)  $13.75\ \text{J}$ , b)  $59.8\ \text{mC}$ .

34) A  $476\ \text{nF}$  capacitor is required to store  $106.8\ \text{mJ}$  of energy. Find:

- a) Potential difference to which the capacitor must be charged.
- b) The charge on the capacitor.

Answer: a)  $670\ \text{V}$ , b)  $318.9\ \mu\text{C}$ .